

QUIZ – ANSWER KEY

QUIZ NO: 59

TOPIC: ELECTRICAL ENGINEERING

DATE: 17/03/2022

1. When a transformer winding suffers a short-circuit, the adjoining turns of the same winding experience
- [A] an attractive force
 - [B] a repulsive force
 - [C] no force
 - [D] none of the above

Answer: A

2. If rated voltage from the power lines is applied to the primary of a single-phase transformer which is operated on load, then
- [A] both input voltage and current are sinusoidal
 - [B] both input voltage and current are non-sinusoidal
 - [C] input voltage is non-sinusoidal and input current is sinusoidal
 - [D] input voltage is sinusoidal and input current is non-sinusoidal

Answer: D

Join our social media



QUIZ – ANSWER KEY

3. “In all cases of electromagnetic induction, an induced voltage will cause a current to flow in a closed circuit in such a direction that the magnetic field which is caused by that current will oppose the change that produces the current” is the original statement of

- [A] Lenz’s law
- [B] Faraday’s law of magnetic induction
- [C] Fleming’s law of induction
- [D] Ampere’s law

Answer: A

4. For successful parallel operation of two single phase transformers, the most essential condition is that their

- [A] percentage impedances are equal
- [B] polarities are properly connected
- [C] turns ratios are exactly equal
- [D] kVA ratings are equal

Answer: B

5. The presence of an uncharged conductor near a charged one increases the

- [A] charge of the charged conductor
- [B] capacity of the charged conductor
- [C] potential of the charged conductor
- [D] all of the above

Answer: B

Join our social media



QUIZ – ANSWER KEY

6. Which of the following statements is correct ?

- [A] Mica capacitors are available in capacitance values of 5 to 20 μF
- [B] Air capacitors have a black band to indicate the outside foil
- [C] Electrolytic capacitors must be connected in correct polarity
- [D] Ceramic capacitors must be connected in correct polarity

Answer: C

7. Two coils having equal resistance but different inductances are connected in series. The time constant of the series combination is the

- [A] the sum of the time constants of the individual coils
- [B] average of the time constants of individual coils
- [C] the geometric mean of the time constants of individual coils
- [D] product of the time constants of individual coils

Answer: B

8. A network contains linear resistors and ideal voltage sources. If the values of all the resistors are doubled, then the voltage across each resistor is

- [A] halved
- [B] doubled
- [C] increased by 4 times
- [D] not changed

Answer: D

Join our social media



QUIZ – ANSWER KEY

9. Two incandescent light bulbs of 40W and 60W rating are connected in series across the mains. Then
- [A] the bulbs together consume 100W
 - [B] the bulbs together consume 50W
 - [C] the 60W bulb glows brighter
 - [D] the 40W bulb glows brighter

Answer: D

10. Double integration of a unit-step function would lead to?
- [A] an impulse
 - [B] a parabola
 - [C] a ramp
 - [D] a doublet

Answer: B

Join our social media

