

QUIZ – ANSWER KEY

QUIZ NO: 83

TOPIC: ELECTRICAL ENGINEERING

DATE: 21/06/2022

1. The secondary of a current transformer is always kept short-circuited while operating because it _____

- [A] Avoids core saturation and high voltage induction
- [B] Is safe to human beings
- [C] Protects the primary circuit
- [D] To keep temperature within limits

Answer: A

2. For a transformer with primary turns 400, secondary turns 100, if 20A current is flowing through primary, we will get _____

- [A] 800A at secondary
- [B] 40A at secondary
- [C] 80A at secondary
- [D] 5A at secondary

Answer: C

Join our social media



QUIZ – ANSWER KEY

3. A 25 KVA transformer is constructed to a turns ratio of $N_1/N_2 = 10$. The impedance of primary winding is $3+j5$ ohms and of secondary winding is $0.5+j0.8$ ohms. What will be the impedance of transformer when referred to primary?

- [A] $53 + 85j$ ohms
- [B] $53j + 85$ ohms
- [C] Can't be calculated
- [D] $3.5 + 5.8j$ ohms

Answer: A

4. The full-load copper loss of a transformer is 1600 W. At half-load, the copper loss will be _____

- [A] 1600 W
- [B] 6400 W
- [C] 400 W
- [D] 800 W

Answer: C

5. Power transformers other than distribution transformers are generally designed to have maximum efficiency around _____

- [A] 10% overload
- [B] Near full-load
- [C] Half-load
- [D] No-load

Answer: B

Join our social media



QUIZ – ANSWER KEY

6. For a power transformer operating at full load it draws voltage and current equal to 200 V and 100 A respectively at 0.8 pf. Iron and copper losses are equal to 120 kW and 300kW. What is efficiency?

[A] 97.44%

[B] 99.12%

[C] 86.44%

[D] 96.44%

Answer: A

7. No-load current in the transformer is _____

[A] Sinusoidal distorted

[B] Sinusoidal

[C] Steps

[D] Straight DC

Answer: A

8. Which of the following is the main advantage of an auto-transformer over a two-winding transformer?

[A] Eddy losses are totally eliminated

[B] Copper losses are negligible

[C] Saving in winding material

[D] Hysteresis losses are reduced

Answer: C

Join our social media



QUIZ – ANSWER KEY

9. For a 20kVA transformer with a turn ratio of 0.4 what amount of total power is transferred inductively?

- [A] 10kVA
- [B] 8kVA
- [C] 50kVA
- [D] 12kVA

Answer: D

10. Which of the following is the major requirement for the transformers used for electronic purposes?

- [A] Constant amplitude voltage gain
- [B] Perfect DC isolation, maximum efficiency and constant voltage gain
- [C] Perfect DC isolation
- [D] Maximum efficiency

Answer: A

Join our social media

