

QUIZ – ANSWER KEY

QUIZ NO: 99

TOPIC: ELECTRICAL ENGINEERING

DATE: 16/08/2022

1. A three-point starter is suitable for ?

- [A] Shunt Motor
- [B] Series Motor
- [C] Shunt & Compound Motor
- [D] Shunt, Series, and compound motor

Answer: C

Explanation:-

3 point starters in DC Shunt and Compound machines serve for the following purposes.

- It limits the high starting current into the armature by having the resistance high at the time of starting and reducing it during the running conditions.
- It also protects the motor from overload and under-voltage conditions.

2. In the DC machine, the fractional pitch winding is used ?

- [A] To reduce the Harmonic in generated EMF

Join our social media



QUIZ – ANSWER KEY

[B] Improve Cooling

[C] Increase EMF

[D] To reduce the copper losses

Answer: A

Explanation:-

- In full pitched coils, as one conductor of a turn in a coil cuts N pole, the other conductor of the same turn cuts S pole resulting in the production of induced emf(E), i.e phase angle is 180 degree
- In short-pitched coils, both conductors of the same turn in a coil don't cut the respective poles simultaneously. so phase angle is slightly less than 180 degree As a result, the magnitude of induced emf gets reduced to $E \times \cos(\alpha/2)$

Where;

$E \times \cos(\alpha/2)$ is called a pitch factor

For eliminating 3rd harmonic from Generated EMF,

$$\cos(3\alpha/2) = 0$$

$$3\alpha/2 = \pi/2$$

$$\alpha = \pi/3 = 60^\circ$$

Join our social media



QUIZ – ANSWER KEY

3. In which of the following applications DC series motor is used ?

- [A] Centrifugal Pump
- [B] Motor Operation in DC and AC
- [C] Water pump drive
- [D] Starter for car

Answer: D

Explanation:-

- In DC series motor Torque (T_a) increases as the Square of armature current (Ia) $T_a \propto I_a^2$.
- So DC motor provides high starting torque which is required to start a car.

4. The number of the pole in Small Dc Motor Up to 5 H.P are ?

- [A] 2 poles
- [B] 4 poles
- [C] 8 poles
- [D] 10 poles

Answer: A

Explanation:-

- Small H.P motors require only 2 poles because as the number of poles is inversely proportional to the speed therefore 2 pole motor runs at high speed than 4 pole motor.
- Two pole motor has better efficiency.
- Two pole motor has better rpm and noise performance.

Join our social media



QUIZ – ANSWER KEY


5. The ratio of starting torque to full load torque is least in ?

- [A] Differential Compound Motor
- [B] Shunt motor
- [C] Series Motor
- [D] Cumulative compound motor

Answer: A

Explanation:-

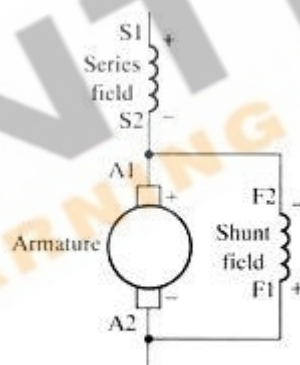- In the differential compound, motor two field windings i.e shunt and series windings oppose each other.
- This causes a reduction in flux and consequences a decrease in torque.



(b) Differential compound dc motor (short shunt)

6. A 220 V, 15 kW, 1000 RPM Shunt Motor with an armature resistance of 0.25Ω , has a rated line current of 68 A and a rated field current of 2.2 A. The change in field flux required to obtain a speed of 1600 RPM while drawing a line current of 52.8 A and a field current of 1.8 A is ?

- [A] 18.18% Increase
- [B] 18.18% decrease

Join our social media



QUIZ – ANSWER KEY

[C] 36.36 % increase

[D] 36.36 % decrease

Answer: D

Explanation:-

Given Data;

Supply Voltage $V = 220\text{ V}$


Speed $N_1 = 1000\text{ RPM}$

Armature Resistance $R_a = 0.25\ \Omega$

Line Current $I_L = 68\text{ A} \ \& \ 52.8\text{ A}$

Field current $I_F = 2.2\text{ A} \ \& \ 1.8\text{ A}$

Speed $N_2 = 1600\text{ RPM}$

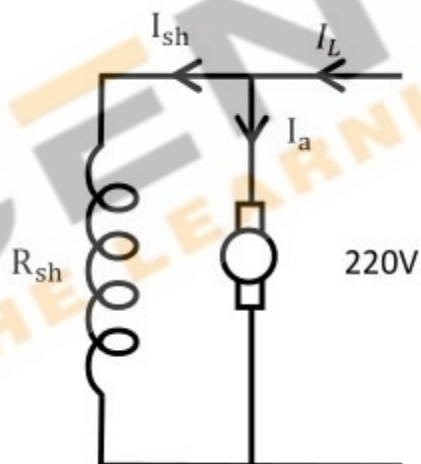

The Line current of DC shunt motor is the sum of Armature current and Shunt field current

$$I_L = I_a + I_{sh}$$

Join our social media



QUIZ – ANSWER KEY

$$\therefore I_a = I_L - I_{sh}$$

$$I_{a1} = 68 - 2.2 = 65.8 \text{ A}$$

From the voltage equation, the Back EMF will be

$$E_{b1} = V - I_{a1}R_a$$

$$= 220 \times 65.8 \times 0.25$$

$$E_{b1} = 203.55$$

Similarly for the line current of 52.8 A and a field current of 1.8 A the armature current will be

$$I_{a2} = 52.8 - 1.8 = 51 \text{ A}$$

$$\text{Hence } E_{b2} = V - I_{a2}R_a$$

$$= 220 \times 51 \times 0.25$$

$$E_{b2} = 207.25$$

Let the on load speed be **N**. As we know that back EMF of DC motor is directly proportional to the flux and speed.

$$E_b \propto N\phi$$

$$E_{b1}/E_{b2} = (N_1/N_2) \times (\Phi_1/\Phi_2)$$

$$203.55/207.25 = (1000/1600) \times (\Phi_1/\Phi_2)$$

$$\Phi_2/\Phi_1 = 0.6364$$

Join our social media



QUIZ – ANSWER KEY

$$\therefore \% \text{ Decrease} = [(\Phi_1 - \Phi_2) / \Phi_1] \times 100$$

$$= 1 - (\Phi_2 / \Phi_1) = 1 - 0.6364 = 0.3636 \times 100 = 36.36$$

7. A separately excited DC motor has an armature resistance of 0.5 W. It runs from a 200 V DC supply drawing an armature current of 20 A at 1500 rpm. For the same field current, the torque developed for an armature current of 10 A will be ?

- [A] 23.59 N-m
- [B] 34.76 N-m
- [C] 15.28 N-m
- [D] 19.99 N-m

Answer: C

Explanation:-

Given parameters;

$$R_a = 0.5 \text{ ohm}$$

$$\text{Supply Voltage } V = 250 \text{ V}$$

$$\text{Armature current } I_a = 20 \text{ A}$$

$$\text{Speed } N = 1500 \text{ rpm}$$

$$\text{Armature current } I_a = 20 \text{ A}$$

$$\text{Torque } T = ?$$

From the voltage equation, the back EMF of DC motor is;

$$E_b = V - I_a R_a$$

$$= 250 - 20 \times 0.5$$

Join our social media



QUIZ – ANSWER KEY

$$E_b = 240$$

The torque of DC motor is

$$T = P / \omega$$

Where;

P = Output power of separately excited motor and it is given as $P = E_b I_a$

ω = Angular speed in rad/sec. and it is given as $\omega = 2\pi N / 60$

Hence for the armature current of 10 A the torque developed is;

$$T = E_b I_a \times 60 / 2\pi N$$

$$= 240 \times 10 \times 60 / 2\pi \times 1500$$

$$= 15.28 \text{ N-m}$$

8. A separately excited 300 V DC shunt motor under no-load runs at 900 rpm drawing an armature current of 2 A. The armature resistance is 0.5Ω and the leakage inductance is 0.01 H. When loaded, the armature current is 15 A. Then the speed in rpm is ?

[A] 881 RPM

[B] 780 RPM

[C] 1000 RPM

[D] 1200 RPM

Answer: A

Explanation:-

Given Data;

Join our social media



QUIZ – ANSWER KEY

Supply Voltage $V = 300 \text{ V}$

No-Load Speed $N_o = 900 \text{ RPM}$

Armature current at no-load $I_a = 2 \text{ A}$

Armature Resistance $R_a = 0.5 \Omega$

Leakage Inductance = 0.01 H

Armature current at full load $I_o = 15 \text{ A}$

⇒ From the voltage equation, the back EMF of DC motor at no-load

$$E_{bo} = V - I_a R_a$$

$$= 300 \times 2 \times 0.5$$

$$E_{bo} = 299 \text{ V}$$

⇒ The back EMF of DC motor on Loaded

$$E_b = V - I_a R_a$$

$$= 300 \times 15 \times 0.5$$

$$E_b = 292.5 \text{ V}$$

Let the on load speed be N . As we know that back EMF of DC motor is directly proportional to the flux and speed.

$$E_b \propto N\phi$$

$$E_b \propto N \text{ (}\phi \text{ is constant)}$$

The ratio of emf and speed can be equated at on load and no-load condition.

$$N/N_o = E_b/E_{bo}$$

Join our social media



QUIZ – ANSWER KEY

$$N = (E_b / E_{b0}) \times N_0$$

$$N = (292.5 / 299) \times 900$$

$$N = 881 \text{ RPM}$$

CENTRE  **C**
THE LEARNING CENTRE

Join our social media



QUIZ – ANSWER KEY

9. A 240 V DC series motor takes 40 A when giving its rated output at 1500 rpm. Its resistance is 0.3 Ω . The value of resistance that must be added to obtain rated torque at 1000 rpm is ?

- [A] 6 Ω
- [B] 5.7 Ω
- [C] 2.2 Ω
- [D] 1.9 Ω

Answer: D

Explanation:-

Supply Voltage $V = 300$ V

Rated Speed $N_1 = 1500$ RPM

Armature current at no-load $I_a = 40$ A

Armature Resistance $R_a = 0.3$ Ω

$N_2 = 1000$ RPM

As it is known the torque is constant, thus armature current and flux will also remain constant. The voltage equation can be given as;

$$E_b = V - I_a R_a$$

$$= 250 - 40 \times 0.3$$

$$E_b = 228$$
 V

At constant flux;

$$N/N_o = E_b/E_b_o$$

$$E_b_2 = (N_2/N_1) \times E_b_1 = (1000/1500) \times 228$$

Join our social media



QUIZ – ANSWER KEY

$$E_b = 152V$$

Now the Back EMF of DC series Motor is given by;

$$E_b = V - I_a(R_a + R_{se})$$

$$152 = 240 - 40(0.3 + R_{se})$$

$$40R_{se} = 76$$

$$R_{se} = 1.9\Omega$$

10. The direction of rotation of a DC shunt motor can be reversed by interchanging ?

- [A] The armature terminal only
- [B] Either field or armature terminals
- [C] The supply terminals
- [D] The field terminals only

Answer: B

Explanation:-

The direction of rotation of a DC shunt motor can be reversed by interchanging the leads of either the field winding or the Armature Winding.

Generally changing the direction of the field is easier, because it carries a lesser current as compared to armature current. However, the reversal should not be done while the armature is excited.

Join our social media

