

## QUIZ – ANSWER KEY

QUIZ NO: 107

TOPIC: ELECTRICAL ENGINEERING

DATE: 20/09/2022

1. If we apply a sinusoidal voltage to a circuit, the product of voltage and current is?

- [A] true power
- [B] apparent power
- [C] average power
- [D] reactive power

**Answer: B**

**Explanation:-**

- If we apply a sinusoidal voltage to a circuit, the product of voltage and current is apparent power. The apparent power is expressed in volt amperes or simply VA.

2. The power factor is called leading power factor in case of \_\_\_\_ circuits ?

- [A] LC
- [B] RC
- [C] RL
- [D] RLC

Join our social media




## QUIZ – ANSWER KEY

Answer: B

Explanation:-

The power factor is called leading power factor in case of RC circuits and not in RLC circuits and RL circuits and LC circuits.

**CENTRE**  **C**  
THE LEARNING CENTRE

Join our social media



## QUIZ – ANSWER KEY

3. A capacitor, used for power factor correction in a single phase circuit decreases which of the following?

- [A] Power factor
- [B] Line current
- [C] Both Line current and Power factor
- [D] Neither Line current nor Power factor

**Answer: B**

**Explanation:-**

We know that a capacitor is used to increase the Power factor. However, with decrease in line current the power factor is increased. Hence line current decreases.

4. A two branch circuit has a coil of resistance  $R_1$ , inductance  $L_1$  in one branch and capacitance  $C_2$  in the second branch. If  $R$  is increased, the dynamic resistance is going to \_\_\_\_\_?

- [A] Increase
- [B] Decrease
- [C] Remains constant
- [D] May increase or decrease

**Answer: B**

**Explanation:-**

- We know that,  
Dynamic resistance =  $L_1/[R_1C_2]$   
So, if  $R_1$  is increased, keeping Inductance and Capacitance same, so The Dynamic resistance will decrease, as the denomination is increasing.

**Join our social media**



## QUIZ – ANSWER KEY

5. For making a capacitor, the dielectric should have \_\_\_\_\_?

- [A] High relative permittivity
- [B] Low relative permittivity
- [C] Relative permittivity = 1
- [D] Relative permittivity neither too high nor too low

**Answer: A**

**Explanation:-**

Relative permittivity is for ideal dielectric which is air. Achieving such a precise dielectric is very difficult.

Low relative permittivity will lead to low value of capacitance.

High relative permittivity will lead to a higher value of capacitance.

6. In a parallel RL circuit, 12 A current enters into the resistor R and 16 A current enters into the Inductor L. The total current I the sinusoidal source is \_\_\_\_\_?

- [A] 25 A
- [B] 4 A
- [C] 20 A
- [D] Cannot be determined

**Answer: C**

**Explanation:-**

Join our social media



## QUIZ – ANSWER KEY

Currents in resistance and inductance are out of phase by  $90^\circ$ .

$$\text{Hence, } I = I_1^2 + I_2^2$$

$$\text{Or, } I = [12^2 + 16^2]^{0.5}$$

$$\text{Or, } I = \sqrt{144 + 256} = \sqrt{400}$$

$$= 20 \text{ A.}$$

7. Consider a series RLC circuit having resistance =  $1\Omega$ , capacitance =  $1 \text{ F}$ , considering that the capacitor gets charged to  $10 \text{ V}$ . At  $t = 0$  the switch is closed so that  $i = e^{-2t}$ . When  $i = 0.37 \text{ A}$ , the voltage across capacitor is \_\_\_\_\_?

[A]  $1 \text{ V}$

[B]  $6.7 \text{ V}$

[C]  $0.37 \text{ V}$

[D]  $0.185 \text{ V}$

**Answer: B**

**Explanation:-**

We know that, during discharge of capacitor,

$$V_C = V_R$$

$$\text{Now, } V_R = 0.67 \times 10 = 6.7 \text{ V}$$

$$\text{So, } V_C = 6.7 \text{ V.}$$

8. A circuit consists of an excitation voltage  $V_s$ , a resistor network and a resistor  $R$ . For different values of  $R$ , the values of  $V$  and  $I$  are as given,  $R = \infty$ ,  $V = 5 \text{ volt}$ ;  $R = 0$ ,  $I = 2.5 \text{ A}$ ; when  $R = 3 \Omega$ , the value of  $V$  is \_\_\_\_\_?

[A]  $1 \text{ V}$

[B]  $2 \text{ V}$

[C]  $3 \text{ V}$

[D]  $5 \text{ V}$

Join our social media



## QUIZ – ANSWER KEY

Answer: C

Explanation:-

When  $R = \infty$ ,  $V = 5\text{v}$ ,

Then,  $V_{oc} = 5\text{V}$  and the circuit is open


When  $R = 0$ ,  $I = 2.5\text{A}$

Then,  $I_{sc} = 2.5$  and the circuit is short circuited.

So,  $R_{eq} = V_{OC}/I_{SC}$

$= 5/2.5 = 2 \Omega$

Hence the voltage across  $3 \Omega$  is 3 volt.

**CENTRE**  **C**  
THE LEARNING CENTRE

Join our social media



## QUIZ – ANSWER KEY

9. Three inductors each 30 mH are connected in delta. The value of inductance or each arm of equivalent star is \_\_\_\_\_ ?

[A] 10 mH

[B] 15 mH

[C] 30 mH

[D] 90 mH

**Answer: A**

**Explanation:-**

We know that if an inductor L is connected in delta, then the equivalent star of each arm =  $LXL/L+L+L$

Given that,  $L = 30 \text{ mH}$

$= 30 \times 30 / 30 + 30 + 30$

$= 900 / 90 = 10 \text{ mH.}$

10. In a series RLC circuit having resistance  $R = 2 \Omega$ , and excited by voltage  $V = 1 \text{ V}$ , the average power is 250 mW. The phase angle between voltage and current is \_\_\_\_\_ ?

[A]  $75^\circ$

[B]  $60^\circ$

[C]  $15^\circ$

[D]  $45^\circ$

**Answer: D**

**Explanation:-**

Join our social media



## QUIZ – ANSWER KEY

$$VI \cos \theta = 0.25 \text{ or } I \cos \theta = 0.25$$

$$\text{Or, } Z \cos \theta = 2$$

$$\text{Or, } V/I \cos \theta = 2$$

$$\text{Or, } \cos \theta = 1/\sqrt{2}$$

So, from the above equations,  $\cos \theta = 0.707$  and  $\theta = 45^\circ$ .

**CENTRE**  **C**  
THE LEARNING CENTRE

Join our social media

