

QUIZ – ANSWER KEY

QUIZ NO: 132

TOPIC: ELECTRICAL ENGINEERING

DATE: 07/12/2022

1. Ripple factor of center tapped full wave rectifier is _____ ?

[A] 1.414

[B] 1.21

[C] 1.3

[D] 0.48

Answer: D

Explanation: Ripple factor of a rectifier is the measure of the effectiveness of a power supply filter in reducing the ripple voltage. It is calculated by taking a ratio of RMS AC voltage to DC output voltage. For a center tapped full wave rectifier, it is 0.482.

2. If input frequency is 50Hz then ripple frequency of center tapped full wave rectifier will be equal to _____?

[A] 100Hz

[B] 50Hz

[C] 25Hz

[D] 500Hz

Join our social media



QUIZ – ANSWER KEY

Answer: A

Explanation: Since in the output of center tapped rectifier one half cycle is repeated hence frequency will be twice as that of input frequency. That is 100Hz.

3. Transformer utilization factor of a center tapped full wave rectifier is equal to ___ ?

[A] 0.623

[B] 0.678

[C] 0.693

[D] 0.625

Answer: C

Explanation: Transformer utilization factor is the ratio of DC power supplied to the AC rating of the primary winding. The factor indicates the effectiveness of transformer usage by the rectifier. For a center tapped full wave rectifier, it is equal to 0.81 w.r.t the primary winding, 0.57 w.r.t the secondary winding (double of that of a half wave rectifier) and the average value is 0.69.

4. If peak voltage on a center tapped full wave rectifier circuit is 5V and diode cut-in voltage is 0.7, then peak inverse voltage on diode will be ___?

[A] 4.3 V

[B] 10 V

[C] 5.7 V

[D] 9.3 V

Answer: D

Explanation: PIV is the maximum reverse bias voltage that can be applied across a diode in the circuit. If PIV rating of the diode is less than this value, breakdown of diode may occur. For a center tapped full wave rectifier, PIV of diode is $PIV = 2V_m - V_d = 10 - 0.7 = 9.3V$.

Join our social media



QUIZ – ANSWER KEY

5. Efficiency of center tapped full wave rectifier is _____ ?

- [A] 50%
- [B] 81.2%
- [C] 40.6%
- [D] 45.3%

Answer: B

Explanation: Efficiency of a rectifier is the effectiveness of rectifier to convert AC to DC. It is obtained by taking a ratio of DC power output to maximum input power delivered to load. It is usually expressed in percentage. For center tapped full wave rectifier, it is 81.2%.

6. In a center tapped full wave rectifier, the input sine wave is $20\sin 500\pi t$. The average output voltage is ____ ?

- [A] 12.73V
- [B] 6.93V
- [C] 11.62V
- [D] 3.23V

Answer: A

Explanation: The equation of sine wave is in the form $E_m \sin \omega t$.
Therefore, $E_m = 20$
Hence output voltage is $2E_m / \pi$. That is $40 / \pi$.

Join our social media



QUIZ – ANSWER KEY

7. In a center tapped full wave rectifier, the input sine wave is $200\sin 50\pi t$. If load resistance is of $1k$ then average DC power output of half wave rectifier is ____ ?
- [A] 12.56W
 - [B] 16.20W
 - [C] 4.02W
 - [D] 8.04W

Answer: B

Explanation: The equation of sine wave is in the form $E_m \sin \omega t$.
On comparing $E_m = 200$
Power = $\frac{4E_m^2}{\pi^2 R_L} = \frac{800}{\pi^2} \times 1000 = 16.20W$.

8. In a center tapped full wave rectifier, the input sine wave is $250\sin 100\pi t$. The output ripple frequency of rectifier will be ____ ?
- [A] 50Hz
 - [B] 200Hz
 - [C] 100Hz
 - [D] 25Hz

Answer: C

Explanation : The equation of sine wave is in the form $E_m \sin \omega t$.
Therefore, $\omega = 100\pi$ that is, frequency $f = \frac{\omega}{2\pi} = 50Hz$
Since the output of center tapped full wave rectifier have double the frequency of input, output frequency is 100Hz.

Join our social media



QUIZ – ANSWER KEY

9. Transformer utilization factor of a bridge full wave rectifier is equal to ___ ?

- [A] 0.62
- [B] 0.69
- [C] 0.81
- [D] 0.43

Answer: C

Explanation: Transformer utilization factor is the ratio of AC power delivered to load to the DC power rating. This factor indicates effectiveness of transformer usage by rectifier. For bridge full wave rectifier it is equal to 0.81.

10. If peak voltage on a bridge full wave rectifier circuit is 5V and diode cut-in voltage is 0.7, then peak inverse voltage on diode will be ___ ?

- [A] 4.3V
- [B] 5.7V
- [C] 10V
- [D] 5V

Answer: A

Explanation: PIV is the maximum reverse bias voltage that can be appeared across a diode in the circuit. If PIV rating of the diode is less than this Value breakdown of diode may occur. Therefore, PIV rating of diode should be greater than PIV in the circuit. For bridge rectifier PIV is $V_m - V_D = 5 - 0.7 = 4.3$.

Join our social media

