

## QUIZ – ANSWER KEY

QUIZ NO: 137

TOPIC: ELECTRICAL ENGINEERING

DATE: 23/12/2022

1. Solid State Relays (SSRs) have a ?

- [A] coil and contact arrangement
- [B] optocoupler
- [C] scr
- [D] none of the mentioned

**Answer: B**

**Explanation:** Coil and contact arrangement is used in mechanical relays, SSRs have a optocoupler which connects the control circuit to the power circuit via light sensitive devices.

2. The converter circuit which employs turn on and turn off when the voltage and/or current through the device is zero at the instant of switching is \_\_\_\_ ?

- [A] a conventional converter
- [B] a resonant converter
- [C] a zero switching circuit
- [D] none of the mentioned

**Answer: B**

**Explanation:** Resonant converters are used to turn on and turn off when the

[Join our social media](#)



## QUIZ – ANSWER KEY

voltage and/or current through the device is zero at the instant of switching.

3. Induction heating is a \_\_\_\_\_ type of heating ?

- [A] zero frequency
- [B] high frequency
- [C] power frequency
- [D] none of the mentioned

**Answer: B**

**Explanation:** As eddy current is proportional to the square of the supply frequency, induction heating is a high frequency heating.

4. The factors governing the induction heating are ?

- [A] resistivity
- [B] relative permeability
- [C] magnetic field intensity
- [D] all of the mentioned

**Answer: D**

**Explanation:** Induction heating depends on all of the above given factors.

5. The reverse recovery time of a diode is  $t_{rr} = 3 \mu\text{s}$  and the rate of fall of the diode current  $(di/dt) = 30 \text{ A}/\mu\text{s}$ . Determine the storage charge ?

- [A]  $145 \mu\text{s}$
- [B]  $135 \mu\text{s}$
- [C] 0

Join our social media



## QUIZ – ANSWER KEY

[D] none of the mentioned

**Answer: B**

**Explanation:** Storage charge =  $(1/2) \times (di/dt) \times (t_{tr})^2 = 135 \mu s$ .

6. For a SCR, conduction angle is  $120^\circ$  when average on-state current is 20 A. When the conduction angle is halved the earlier value, the on-state average current will be?

[A] 5 A

[B] 40 A

[C] 10 A

[D] 20 A

**Answer: B**

**Explanation:** When the conduction angle is halved, the device will conduct twice then it was conducting earlier. Hence,  $I = 2 \times 20 = 40 \text{ A}$ .

7. A single-phase full bridge diode rectifier delivers power to a constant load current of 10 A. The average and rms values of the source currents will be respectively ?

[A] 5 A, 10 A

[B] 10 A, 10 A

[C] 5 A, 5 A

[D] 10 A, 5A

**Answer: B**

**Explanation:** As the load current is continuous,  $I_{avg} = I_{rms} = 10 \text{ A}$ .

8. TRIAC is used in ?

[A] chopper

[B] speed control of induction machine

Join our social media



## QUIZ – ANSWER KEY

- [C] speed control of universal motor
- [D] none of the mentioned

**Answer: C**

**Explanation:** TRIAC is used in speed control of universal motor.

9. The ratio  $V_{rms}/V_{dc}$  is known as ?

- [A] Form factor
- [B] Ripple factor
- [C] Utilization factor
- [D] None of the mentioned

**Answer: A**

**Explanation:**  $V_{rms}/V_{dc} = \text{Form Factor}$

10. Determine the loss in the snubber circuit, if  $C = 0.545 \mu\text{F}$  and supply is 200 V, 10 kHz ?

- [A] 233 W
- [B] 133 W
- [C] 333 W
- [D] 233 W

**Answer: B**

**Explanation:** Snubber loss  $P_s = (1/2) \times C \times V^2 \times f = 133.1 \text{ W}$

Join our social media

